 


Experiment# 9

Aim: Design of accumulator and basic CPU.

Exercise#1: Design and verify 8-bit logic diagram of accumulator shown Fig. 1 in that performs following operations. Use in built blocks of register as accumulator, 8:1 multiplexer as control (gates) unit, and two 8-bit input pins one as data register (DR) and other as input register (INPR).



Exercise#2: Design and verify 4-bit CPU shown Fig. 3 that performs operations given in Table-2. Use in built blocks of registers, multiplexers and decoder and sub circuit of ALU (designed in experiment no. 6).

